
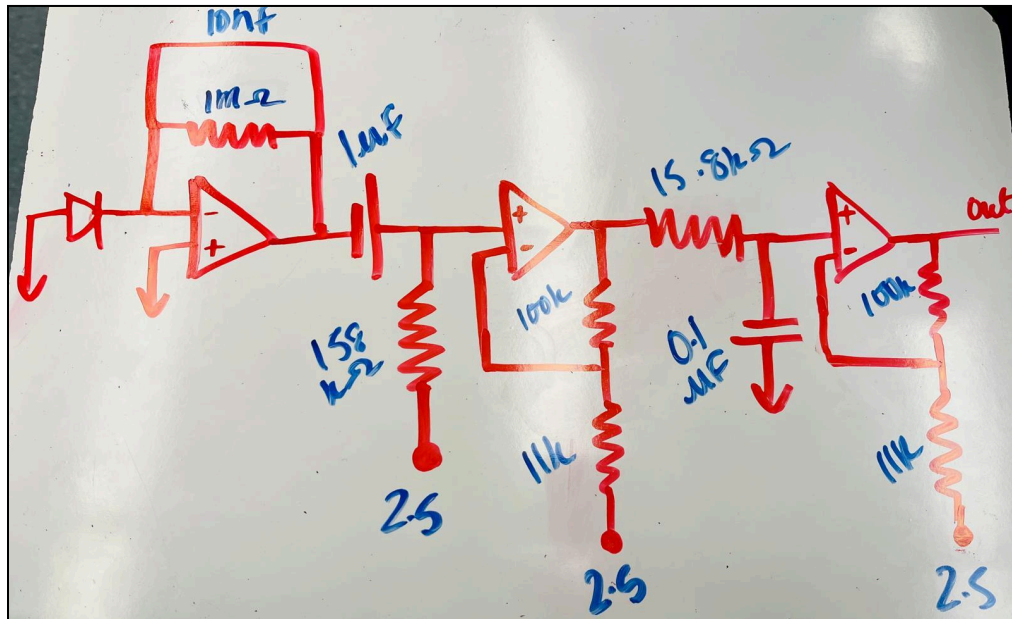


Lab 7- Pulse Oximeter
Kuhu Jayaswal
3rd April, 2025


Circuit Schematic:

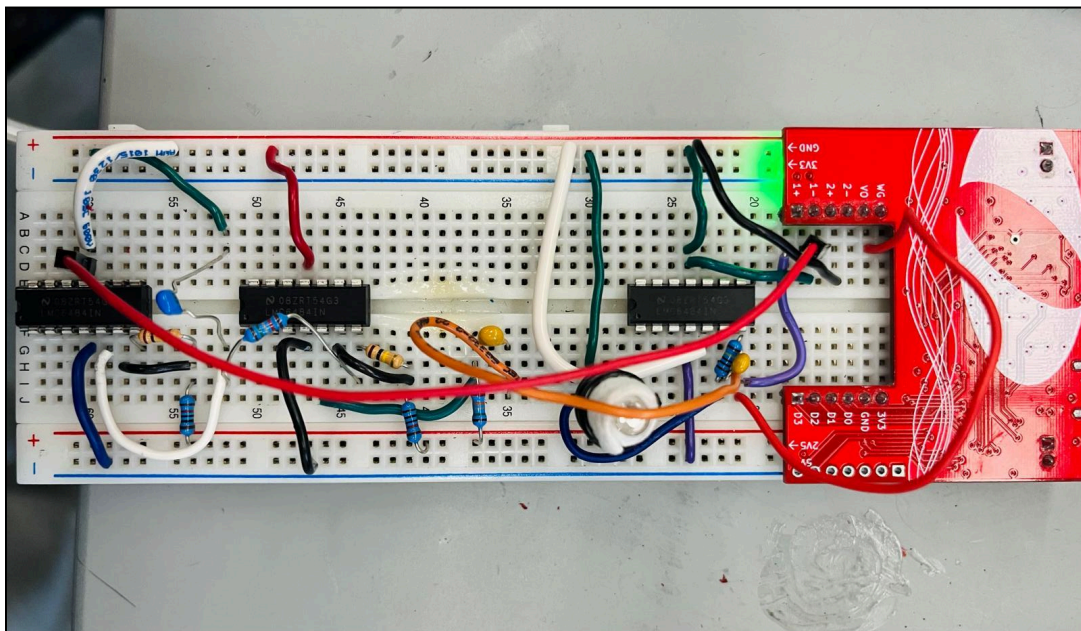

Circuit Picture:



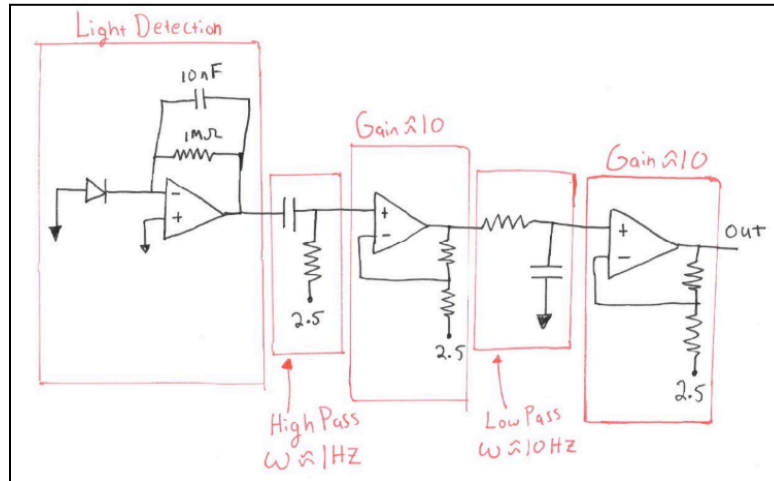Explanation for Resistor & Capacitor Values:



Equations Used:

Cutoff Frequency: $f = 1/2\pi RC$

Gain: $(V_{out}/V_{in}) = \text{gain} * (R_1 + R_2)/R_2$ where $R_1 > R_2$

Using the given schematic from the lab, the process to find the resistor and capacitor values was basically through “plug and chug” and simple substitution of variables.

Note: did the calculations on a whiteboard, but forgot to take pictures sorry!

- High Pass Filter:

$$f = 1 \text{ Hz}, C = 1\mu F \Rightarrow R = 158k\Omega$$


- Low Pass Filter:

$$f = 10 \text{ Hz}, C = 0.1\mu F \Rightarrow R = 15.8k\Omega$$

- Op-Amps (both):


$$V_{in} = 5V, V_{out} = 2.5V, R_1 = 100k\Omega, \text{gain} = 10 \Rightarrow R_2 = 11k\Omega$$

Code Plot:

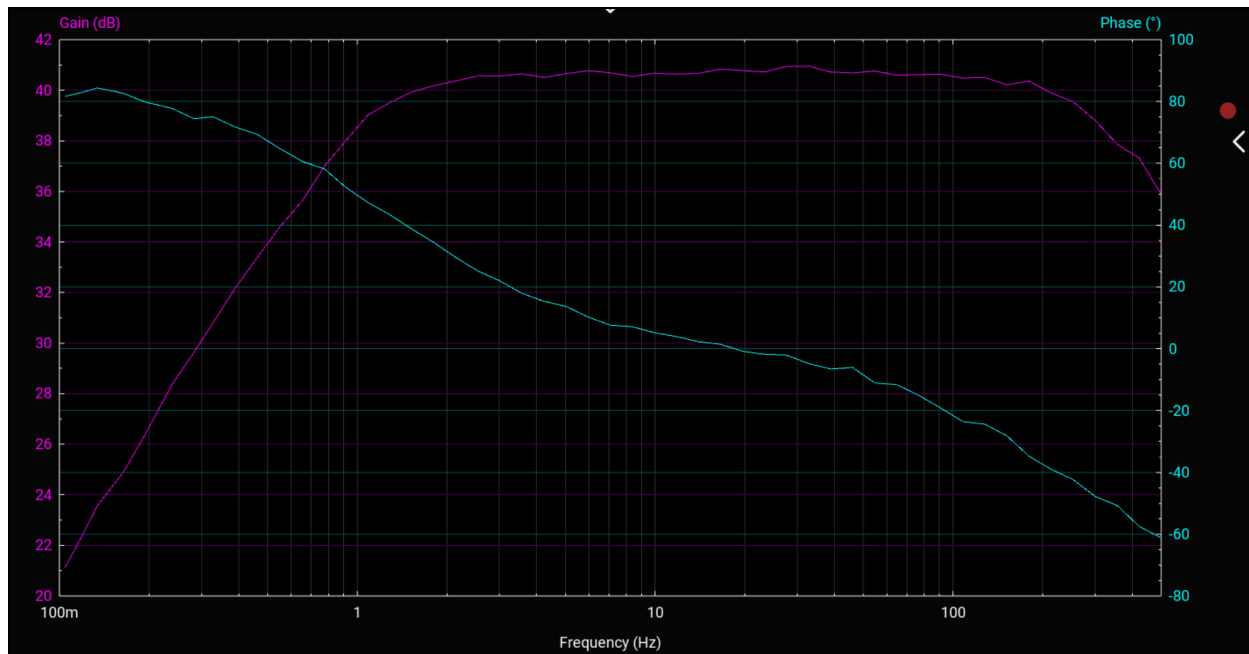

Caption: Gain vs. frequency showing band-pass behavior from ~1 Hz to ~100 Hz, ideal for detecting pulse signals.

Trace of Pulse:

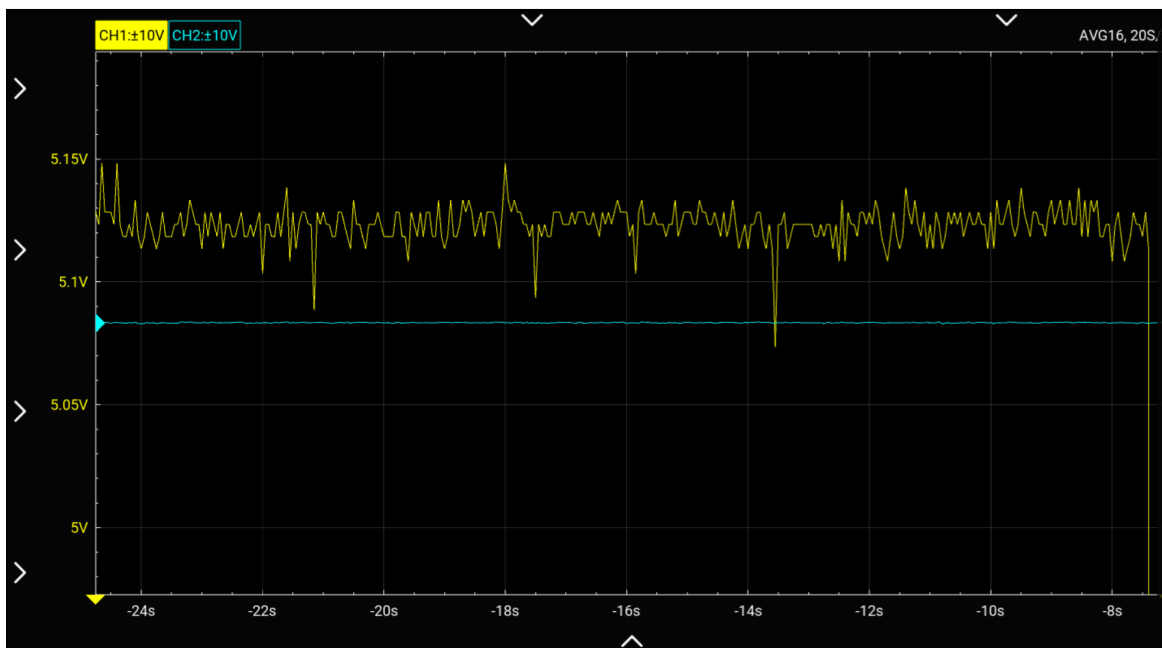

Caption: Voltage signal from finger showing clear pulse waveform after filtering and amplification.